 



Recap: FSM for Vending Machine




Ran out of
specific drink
selection



Recap: Implementing a FSM

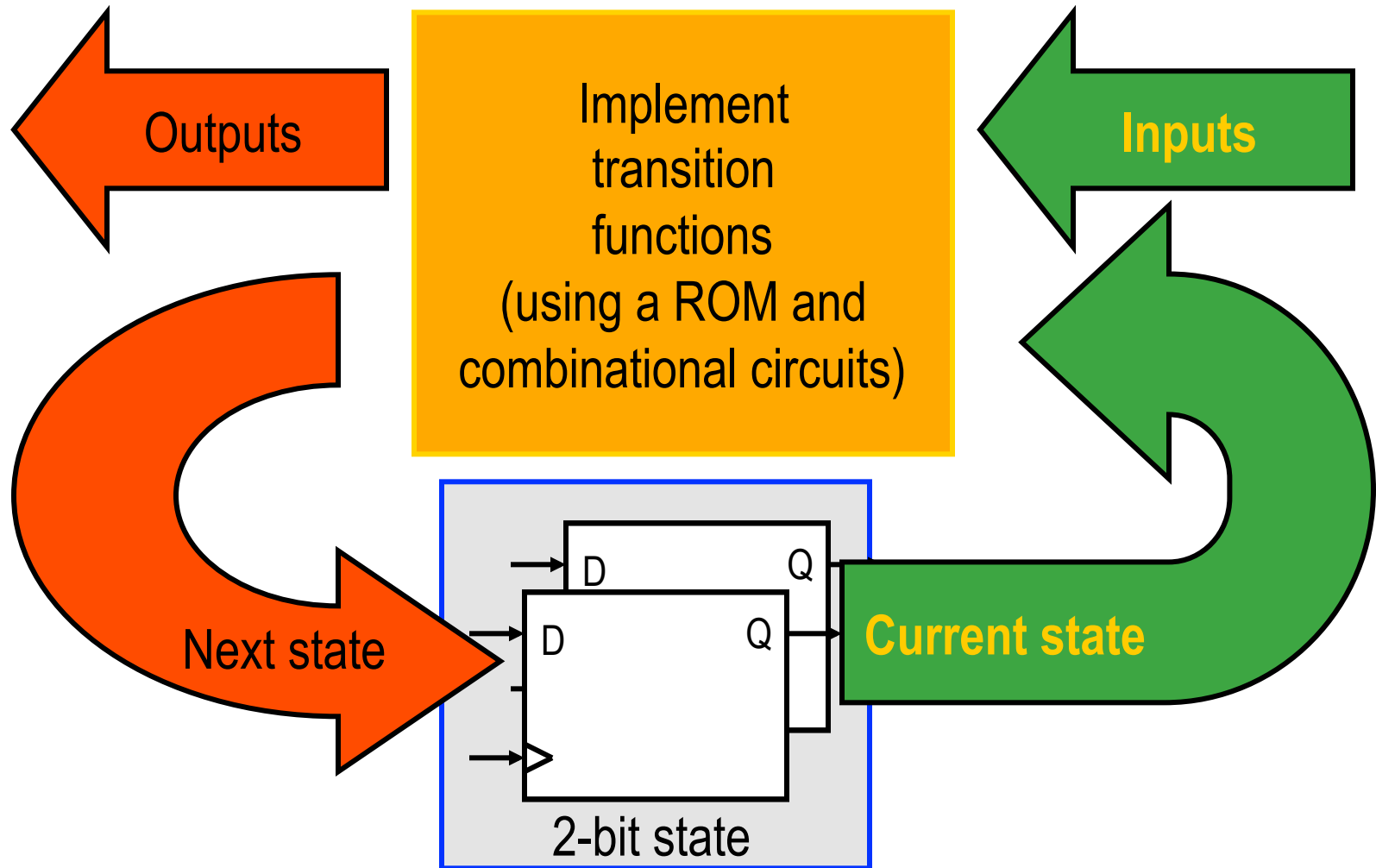

Putting it all together

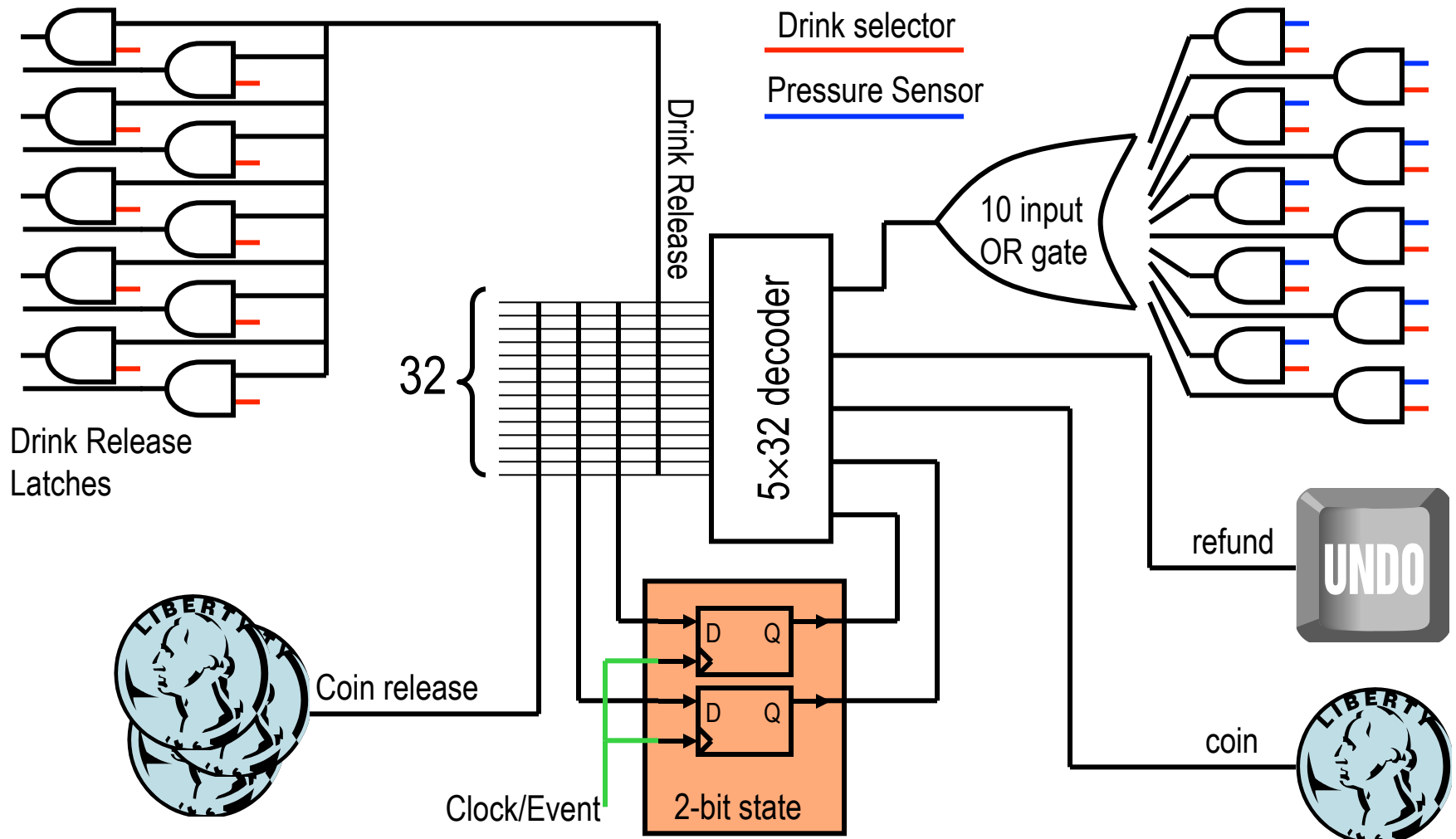

Limitations of the controller


- ❑ What happens if we make the price \$1.00?, or what if we want to accept nickels, dimes and quarters?
 - Must redesign the controller (more state, different transitions)
 - A programmable processor only needs a software upgrade.
 - If you had written really good software anticipating a variable price, perhaps no change is even needed

Single-Cycle Processor Design

❑ General-Purpose Processor Design

- Fetch Instructions
- Decode Instructions
 - Instructions are input to control ROM
- ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
- Clock drives it all
- Single-cycle datapath: Each instruction completes in one clock cycle

LC2Kx Processor as FSM

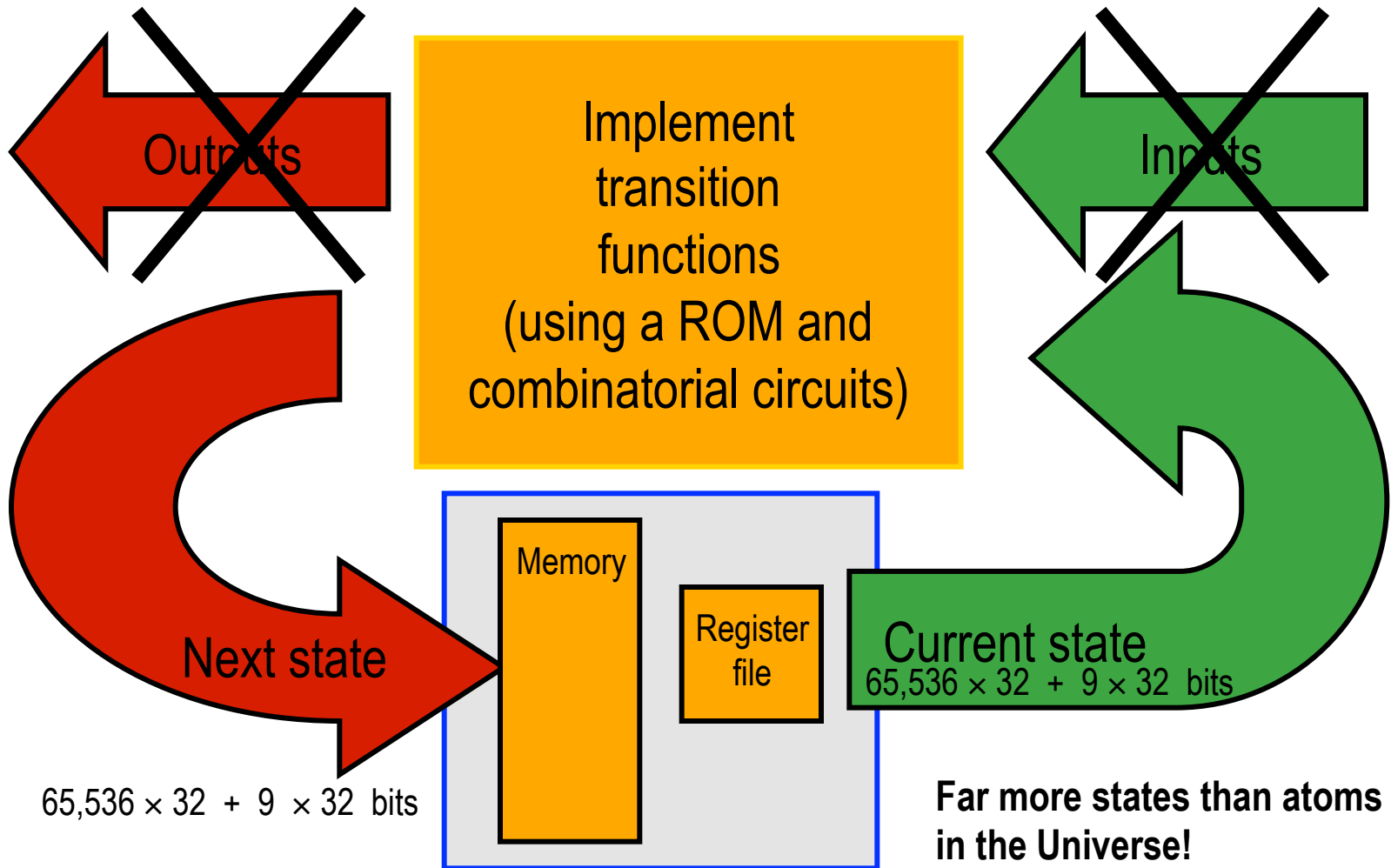


Pentium Processor Die

❑ State


- Registers
- Memory

❑ Control ROM


❑ Combinational logic (Control)

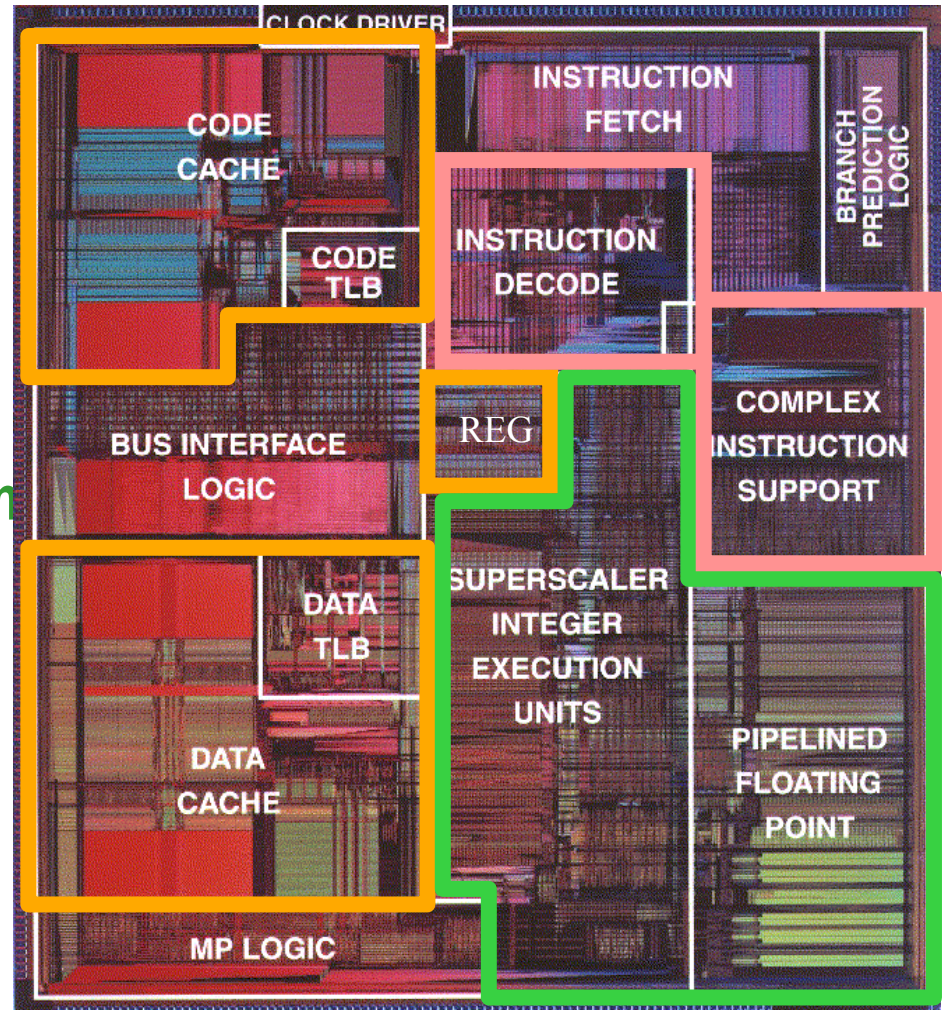


LC2Kx Datapath Implementation

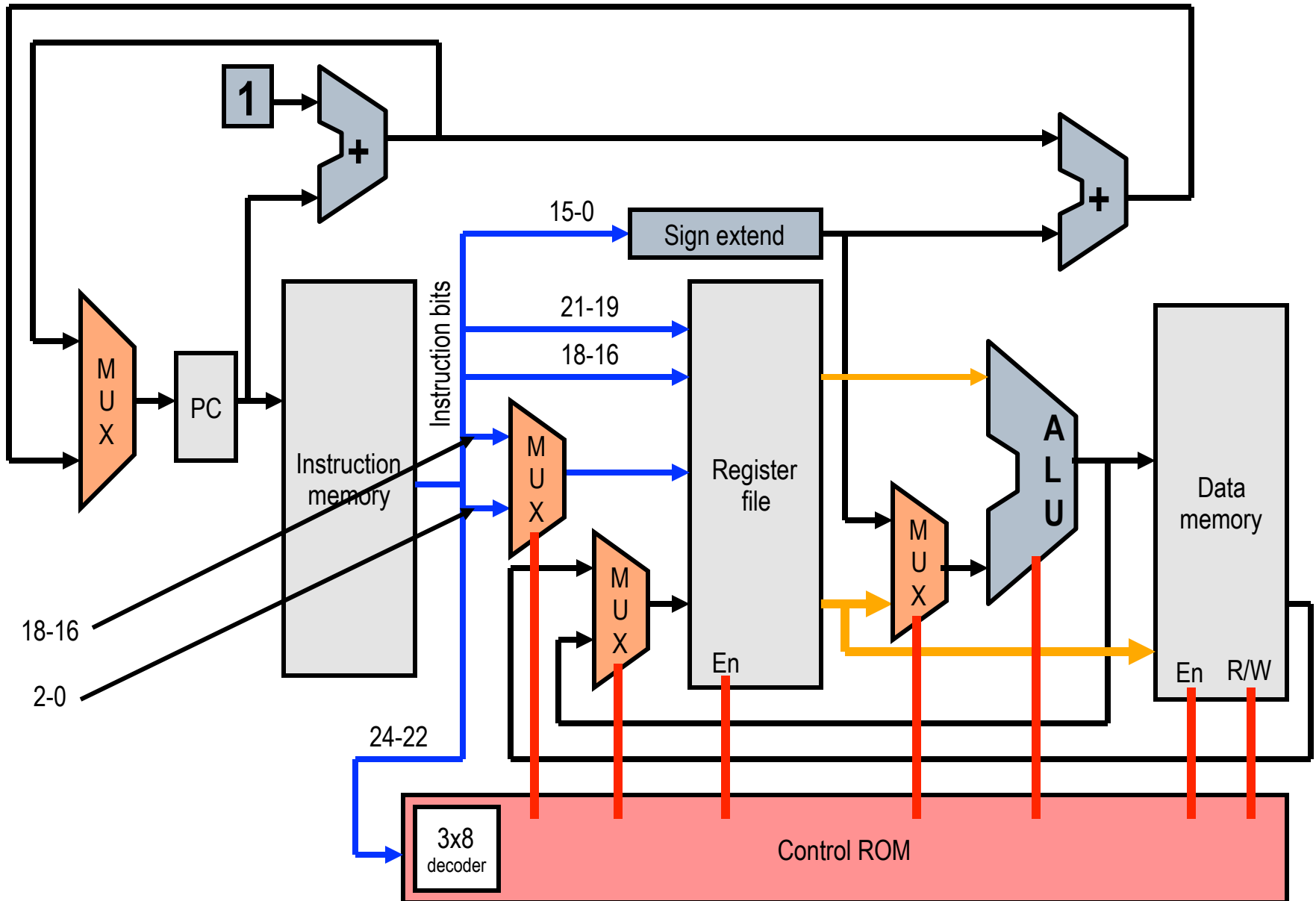

Building Blocks for the LC2

 


State

 


Control

Compute

 

Here are the pieces, go build yourself a processor!


Control Building Blocks (1)

 

Connect one of the inputs to OUT based on the value of select

```
If (select == 0)
    OUT = IN1
Else
    OUT = IN2
```

Control Building Blocks (2)

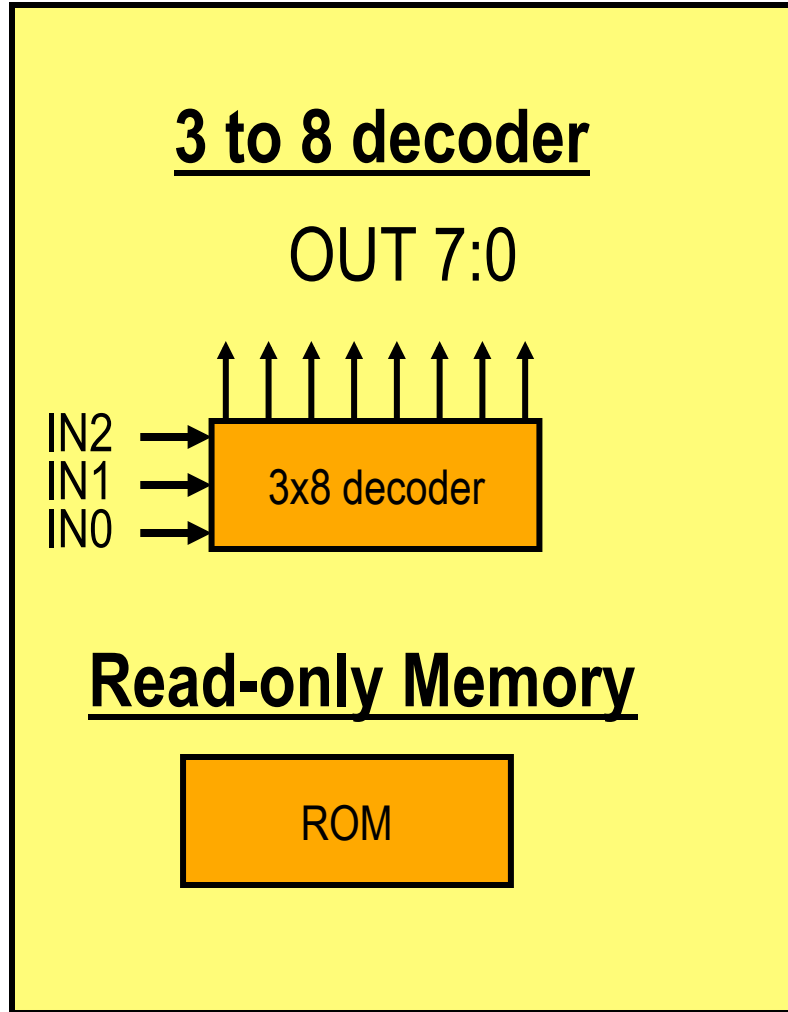


Decoder activates one of the output lines based on the input

IN	OUT
<u>210</u>	<u>76543210</u>
000	00000001
001	00000010
010	00000100
011	00001000
etc.	


ROM just stores preset data in each location.
Give address to access data.

Compute Building Blocks (1)

Arithmetic Logic Unit

 

Adder

 

Perform basic arithmetic functions

$$\text{OUT} = f(\text{IN1}, \text{IN2})$$


$$\text{EQ} = (\text{IN1} == \text{IN2})$$

For LC2, $f = \text{add, nand}$.

For other processors, there are many more functions.

Simple ALU – Does only adds

Compute Building Blocks (2)

 

Sign extend input by replicating the MSB to width of output


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

State Building Blocks (1)

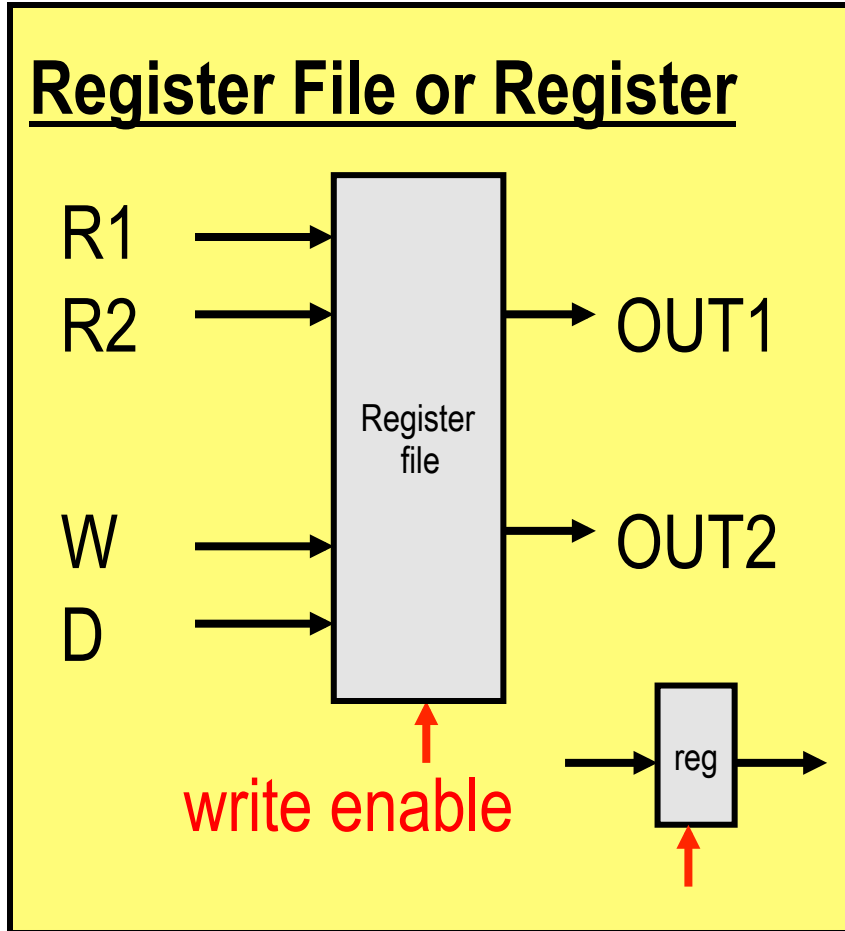

Small/fast memory to store temporary values

n entries (LC2 = 8)

r read ports (LC2 = 2)

w write ports (LC2 = 1)


* R_i specifies register number to read

* W specifies register number to write

* D specifies data to write

How many bits are R_i and W_i in LC2?

State Building Blocks (2)

 


Slower storage structure to hold large amounts of stuff.


Use 2 memories for LC2

- * Instructions
- * Data
- * 65,536 total words


LC2Kx Datapath Implementation

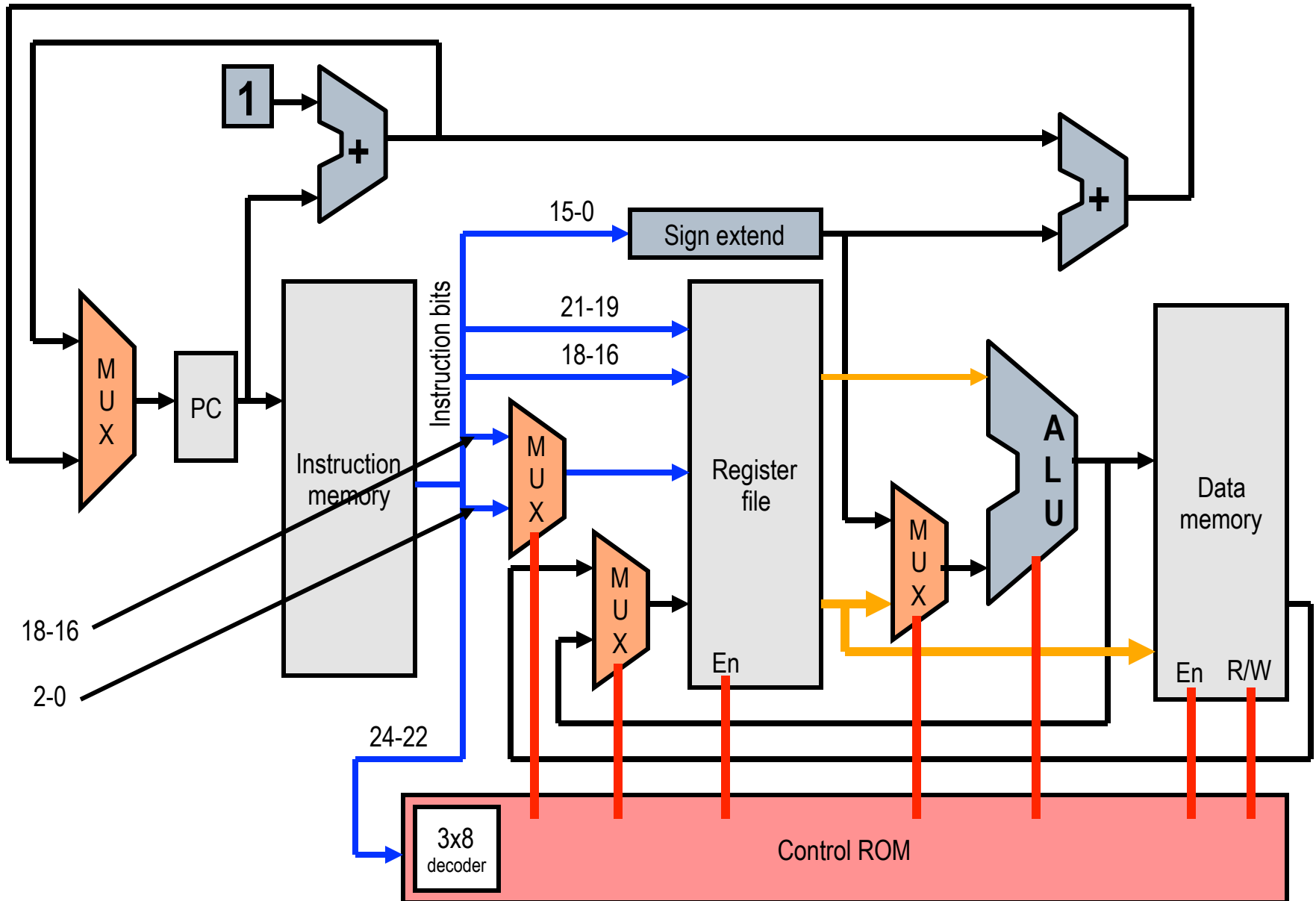


Executing an **ADD** Instruction

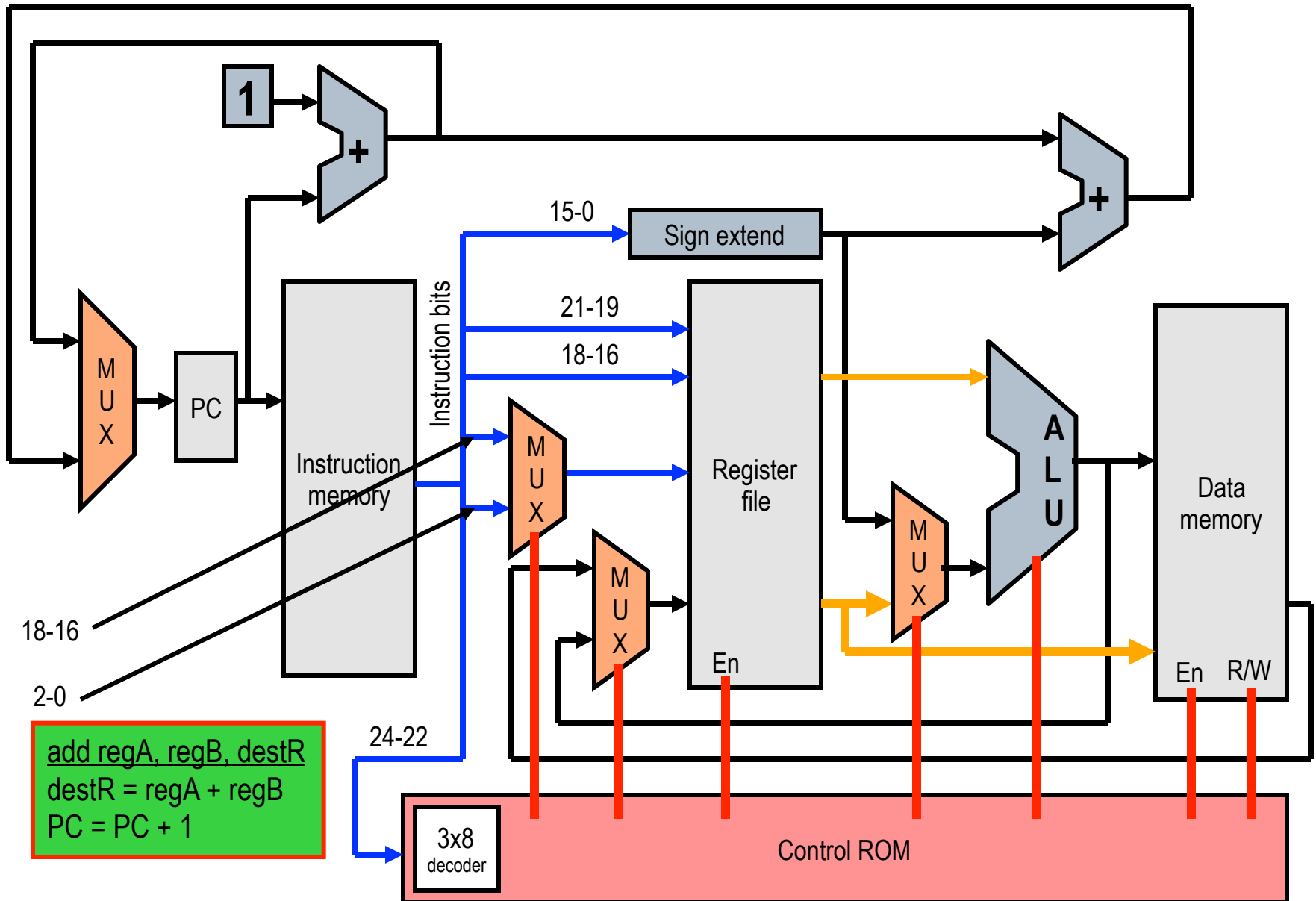

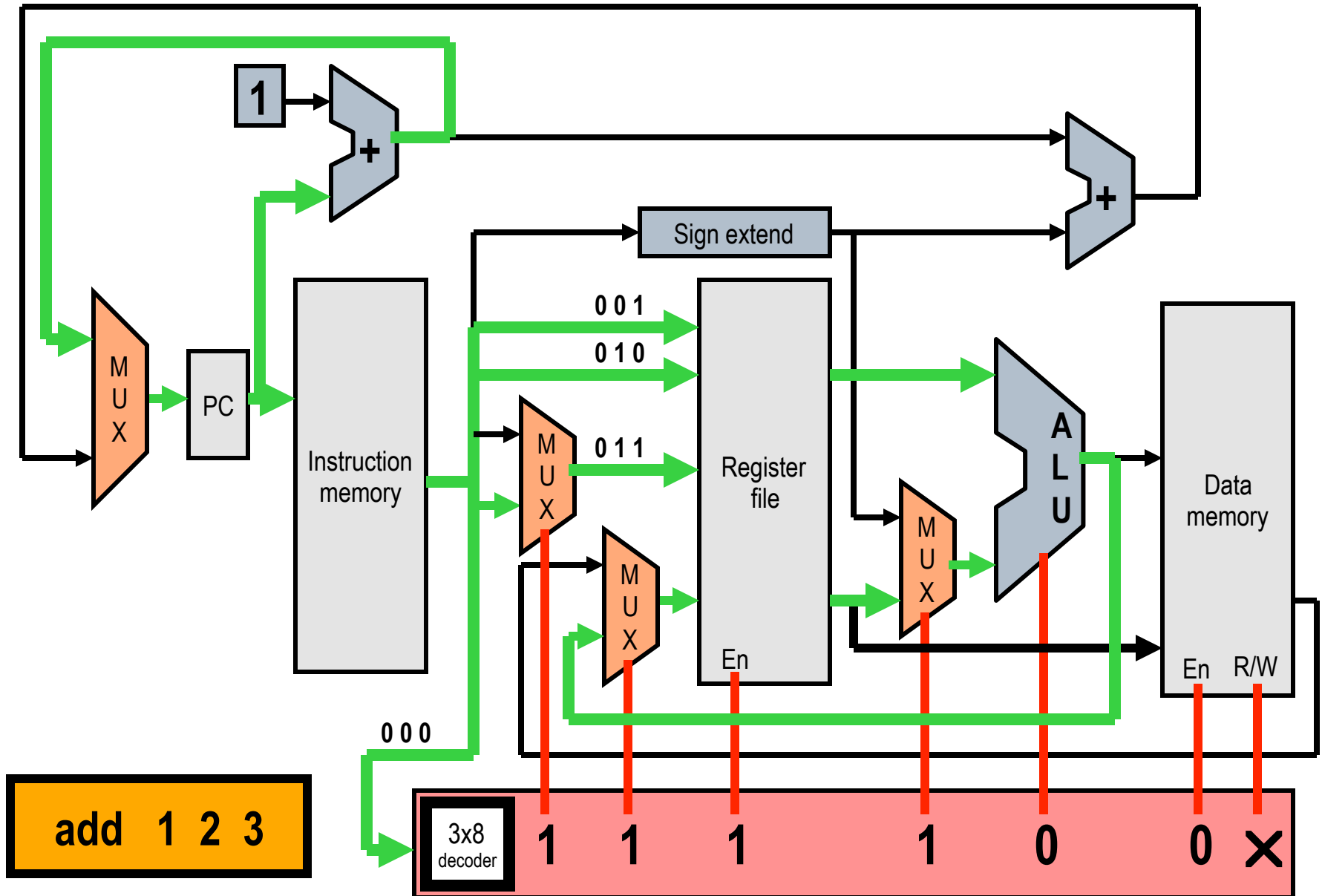
Executing an **ADD** Instruction on LC2Kx Datapath




Executing a **NAND** Instruction

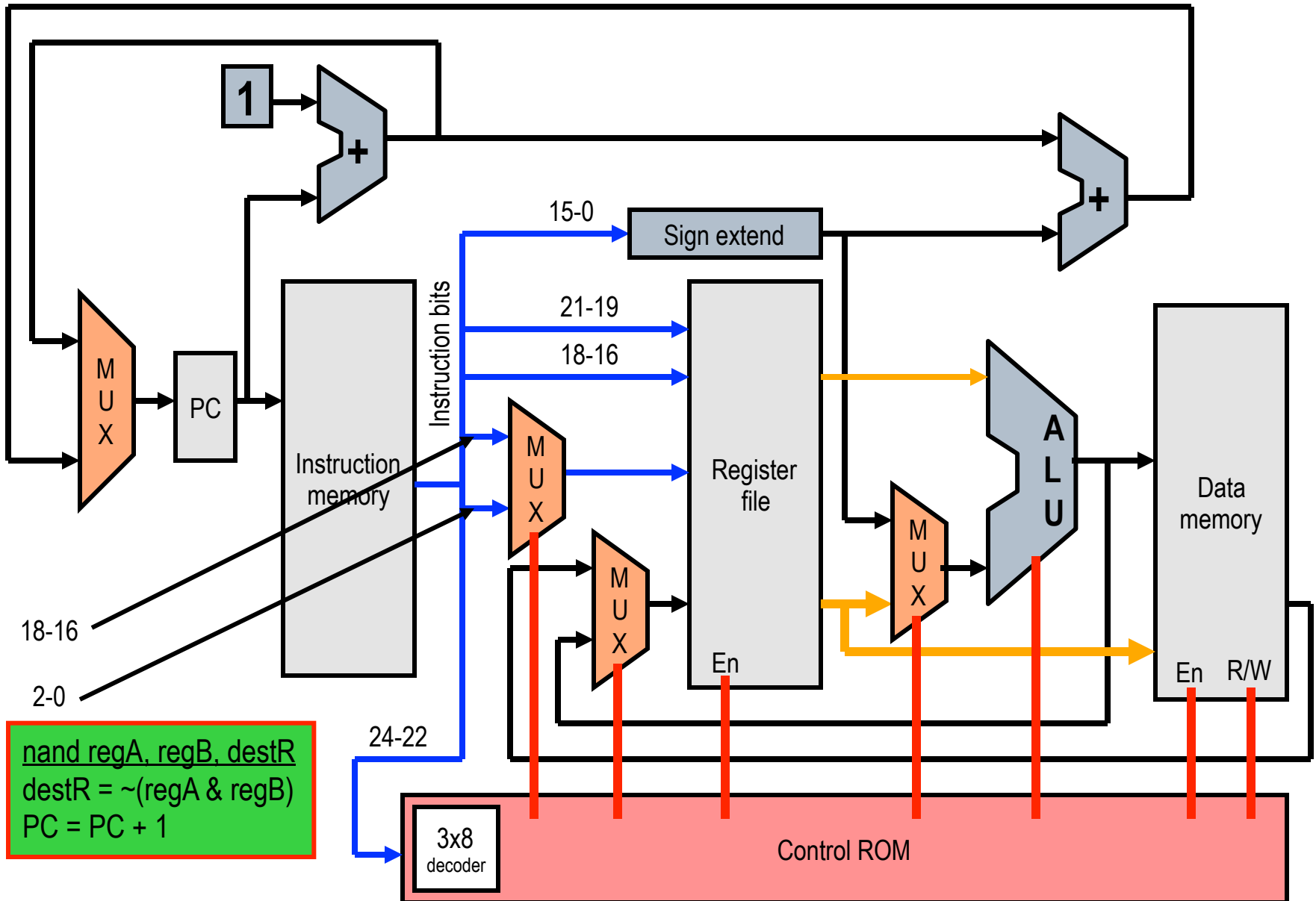

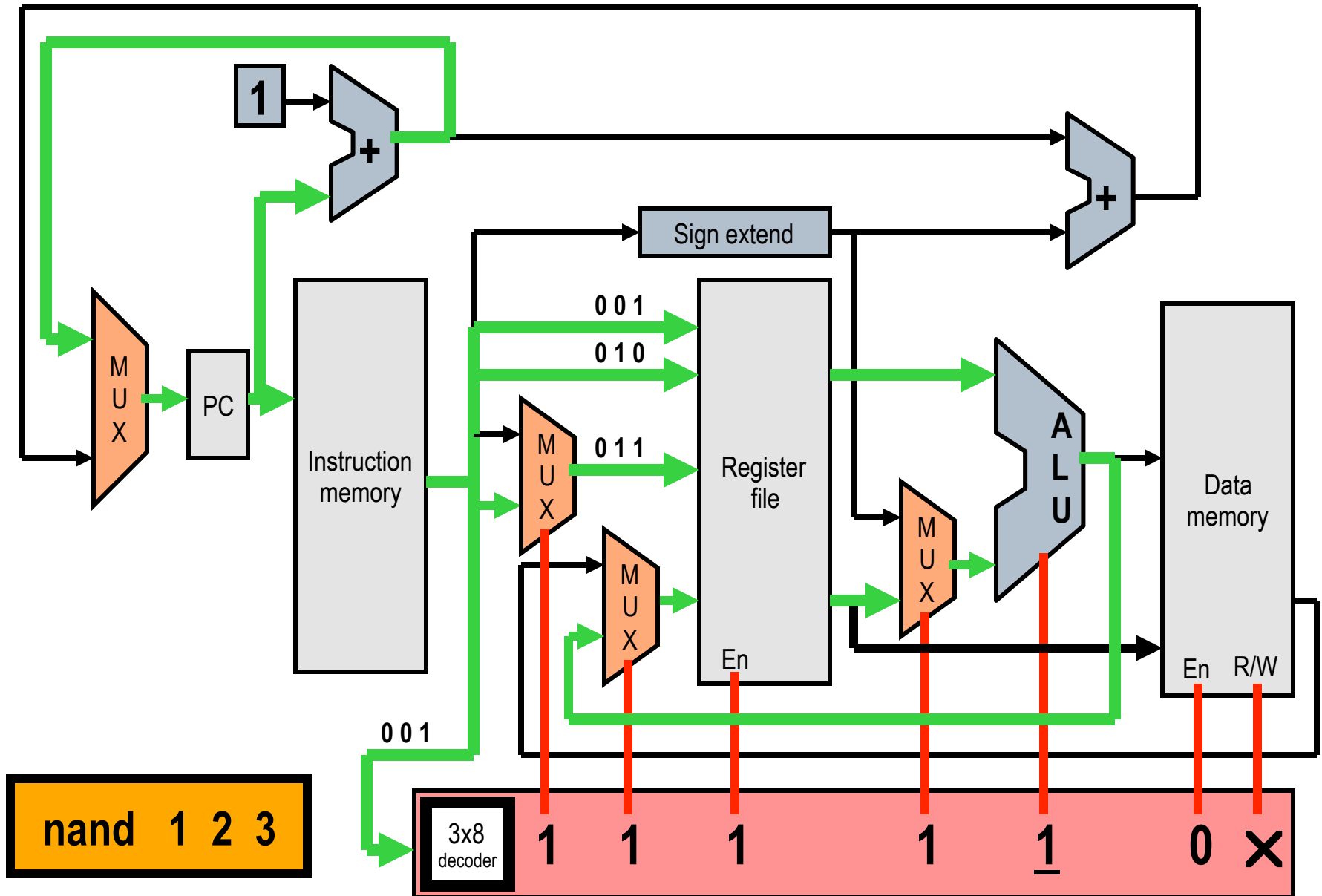Executing **NAND** Instruction on LC2Kx Datapath




Executing a **LW** Instruction

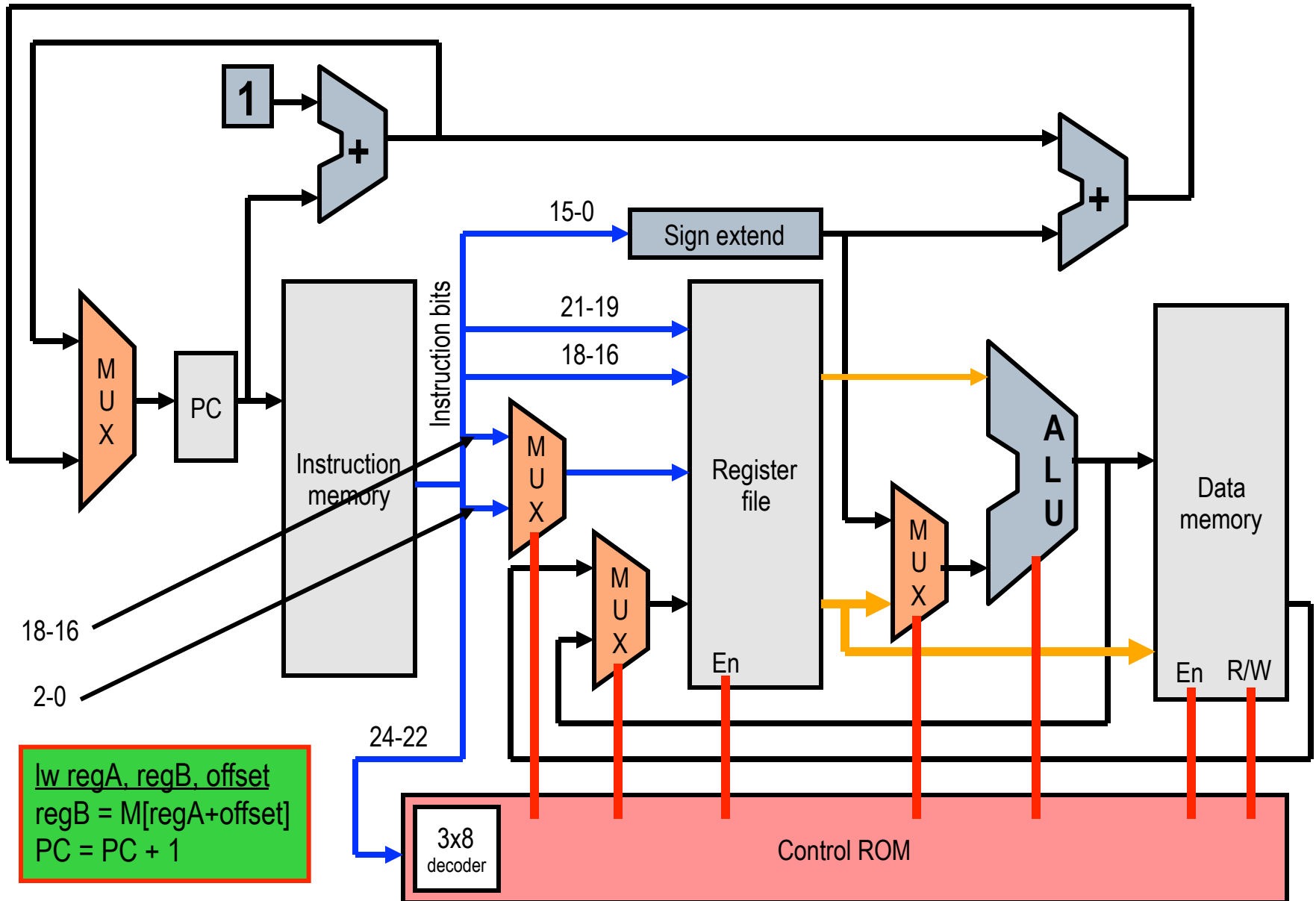


lw regA, regB, offset
regB = M[regA+offset]
PC = PC + 1

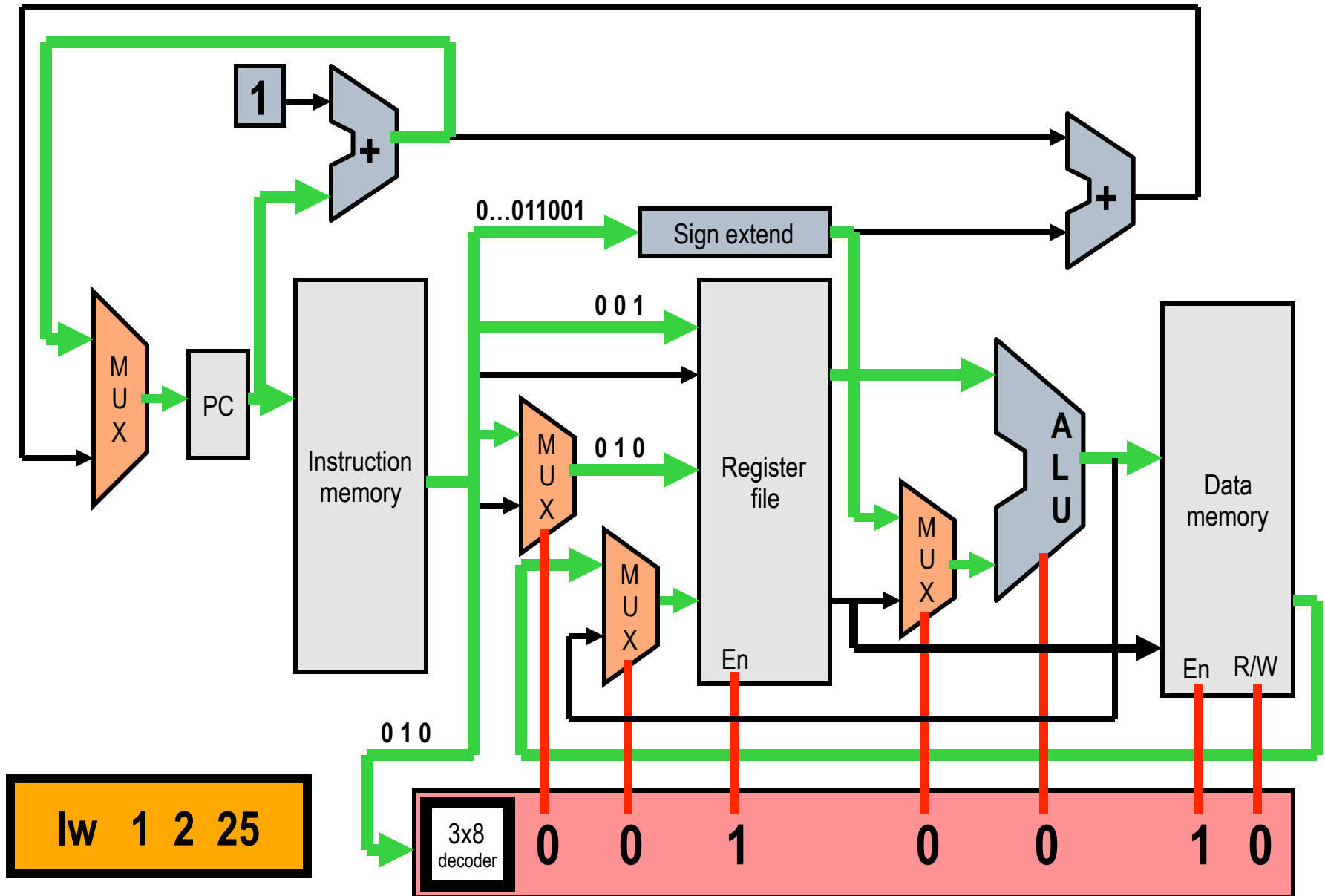
Executing a **LW** Instruction on LC2Kx Datapath




Executing a **SW** Instruction

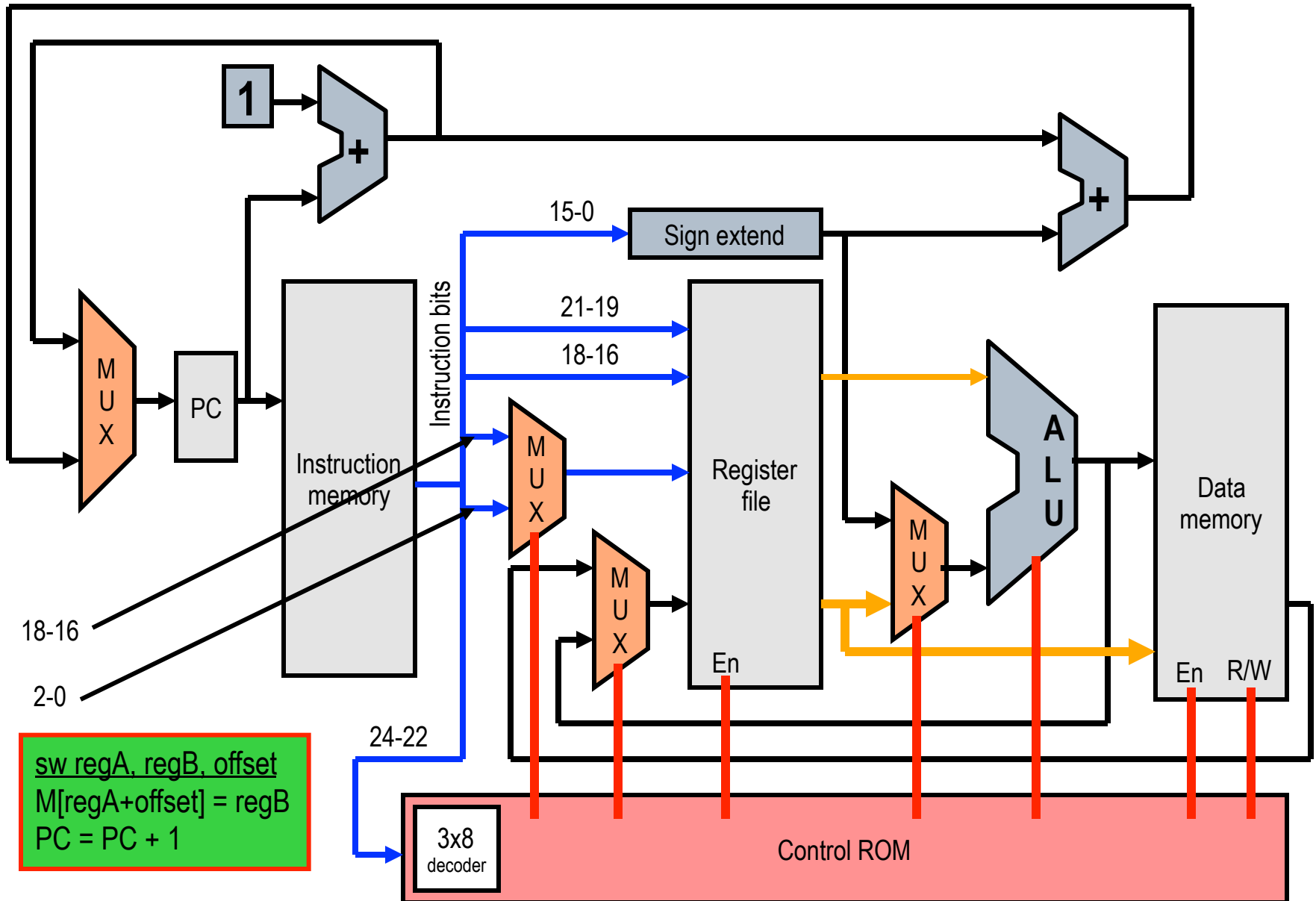

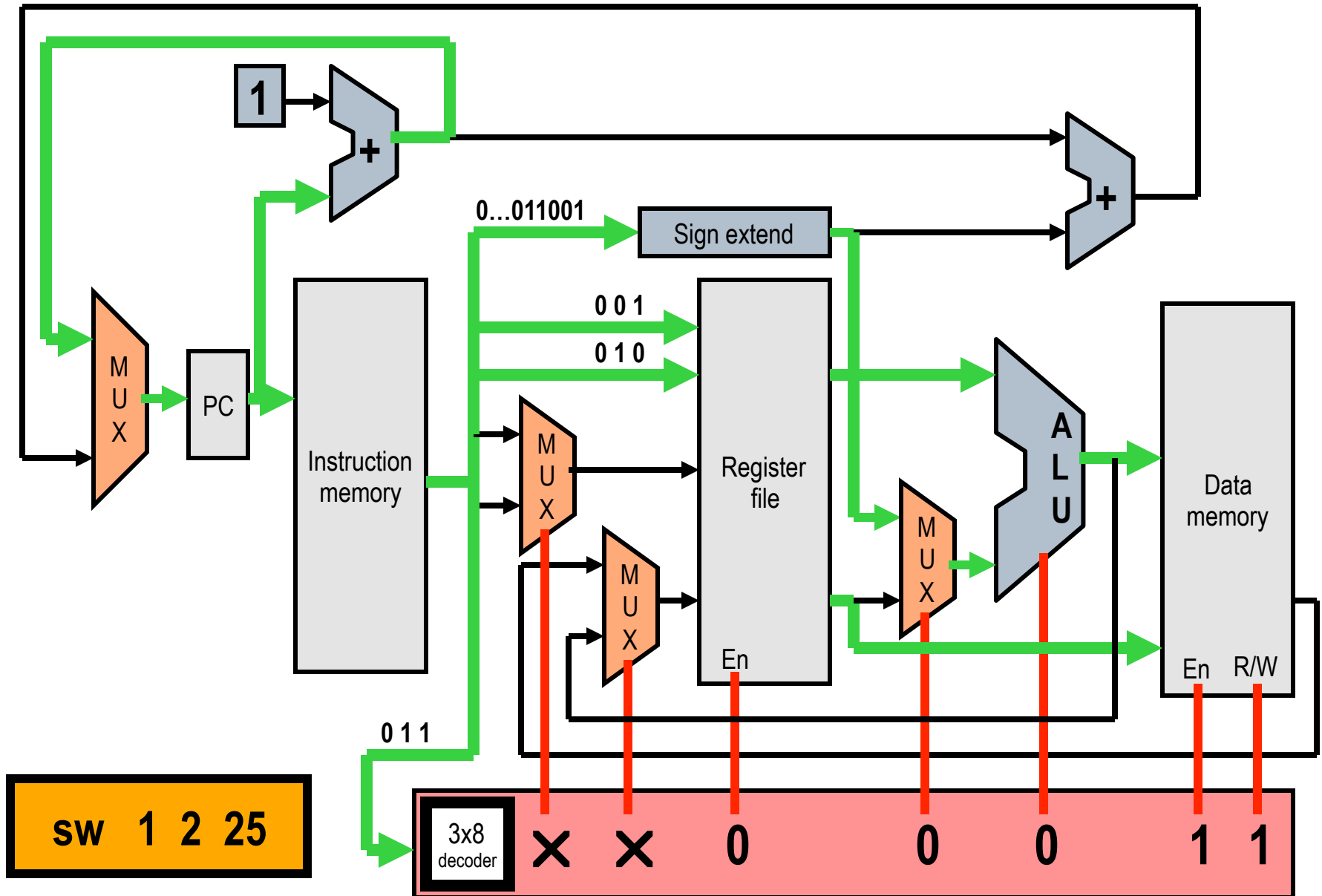
Executing a **SW** Instruction on LC2Kx Datapath




Executing a **BEQ** Instruction

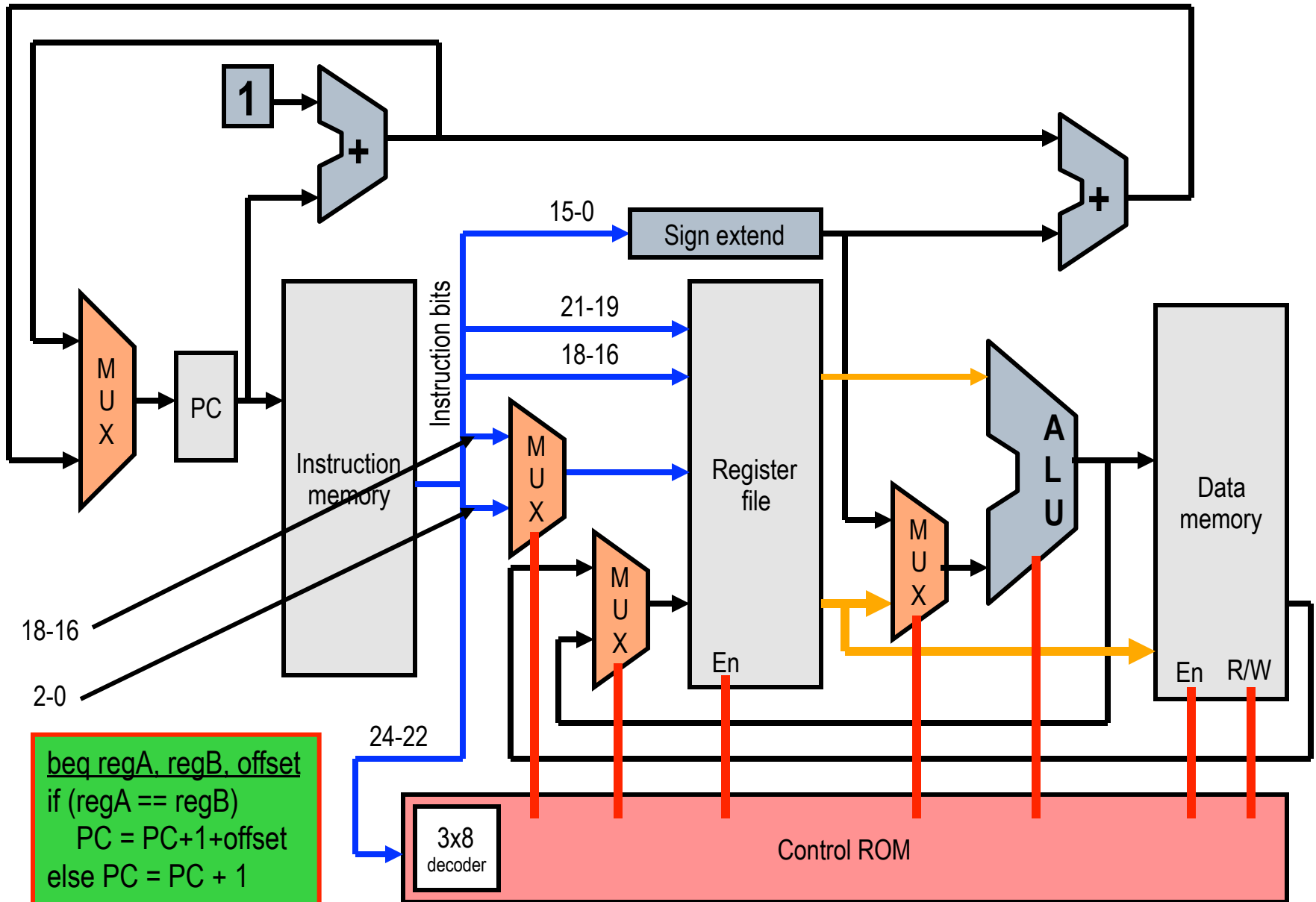

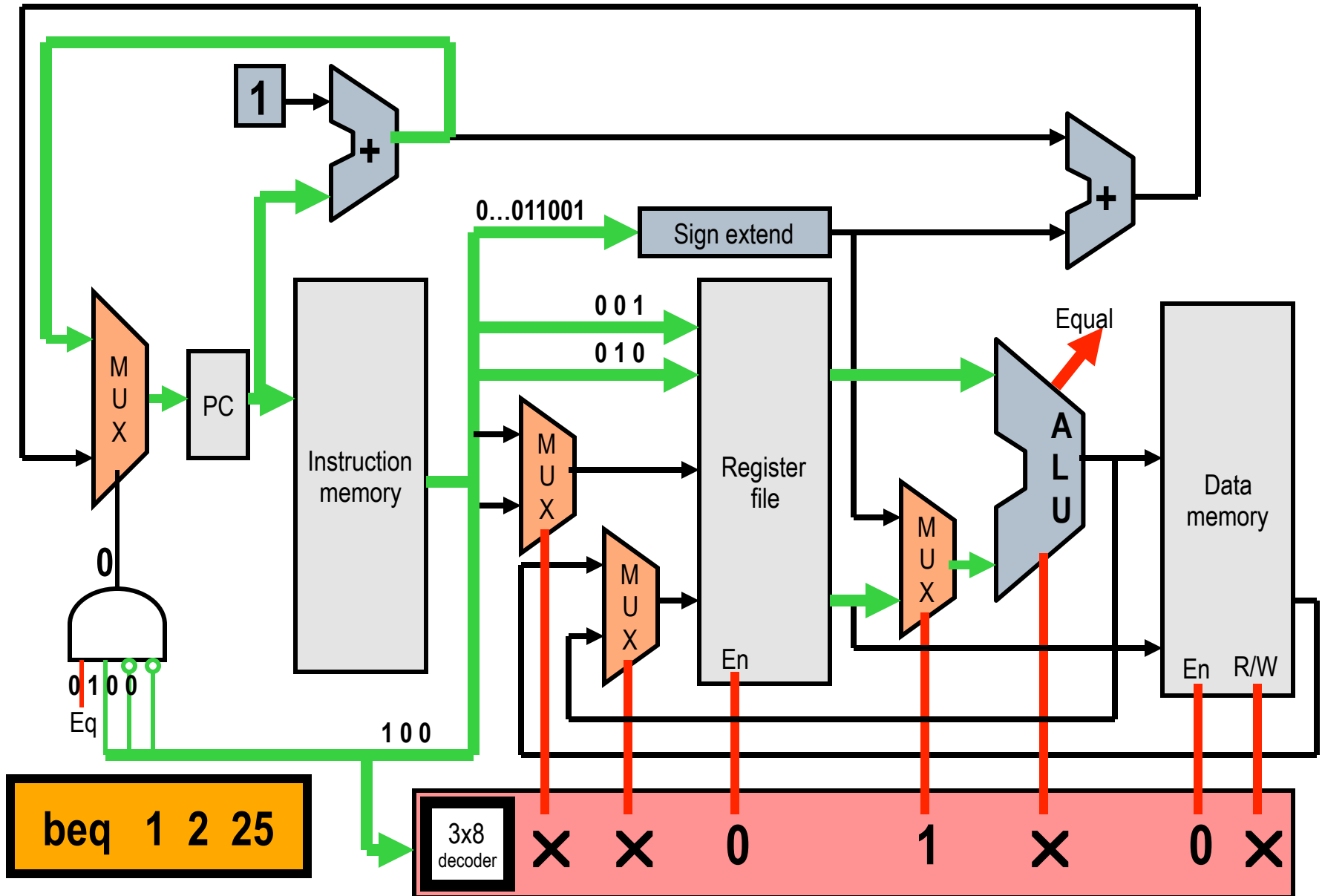Executing a “not taken” **BEQ** Instruction on LC2K Datapath



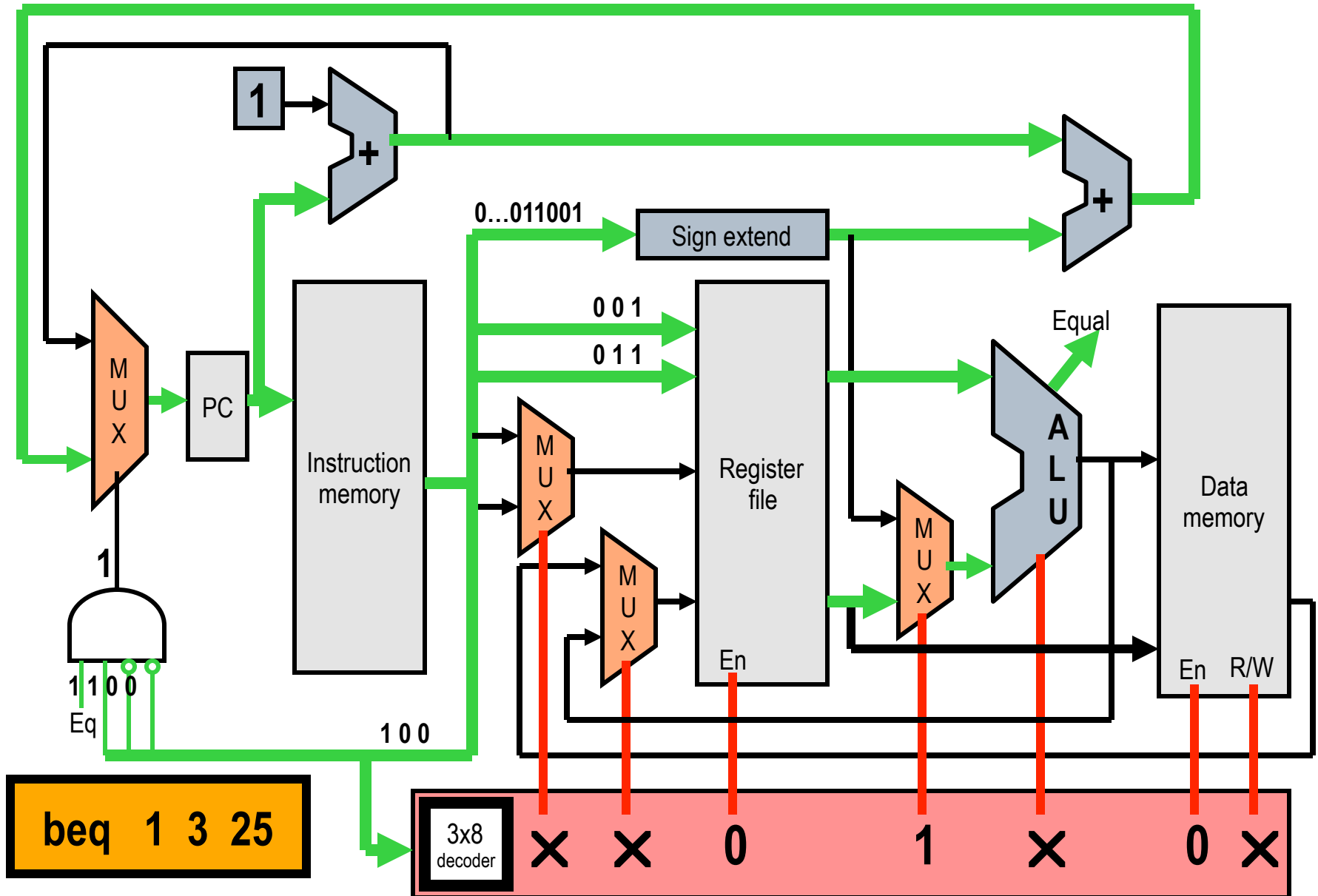Executing a “taken” **BEQ** Instruction on LC2K Datapath



So Far, So Good

❑ Every architecture seems to have at least one ugly instruction.

- JALR doesn't fit into our nice clean datapath


- To implement JALR we need to

- Write PC+1 into regB
- Move regA into PC


- Right now there is:

- No path to write PC+1 into a register
- No path to write a register to the PC


Executing a JALR Instruction

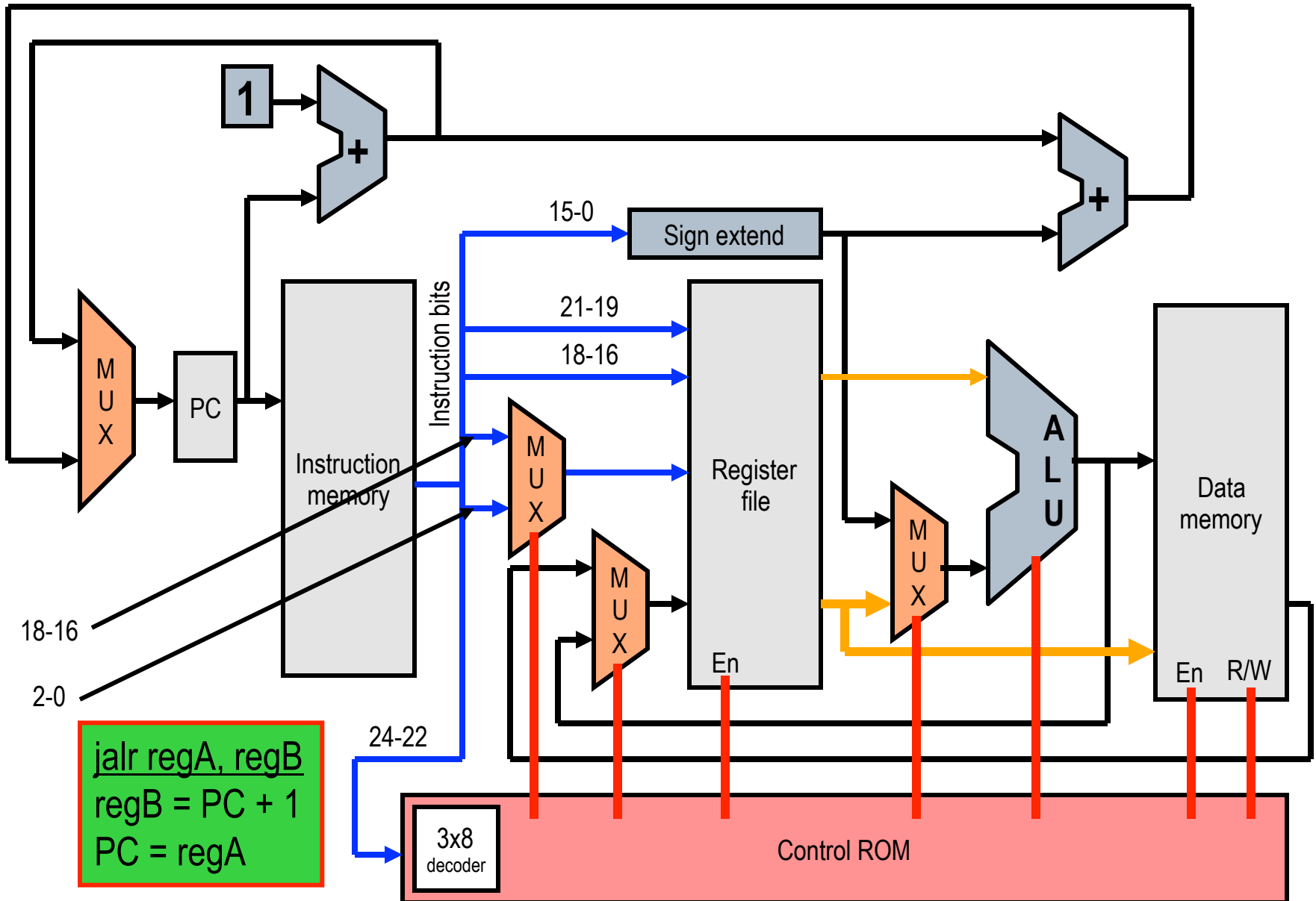

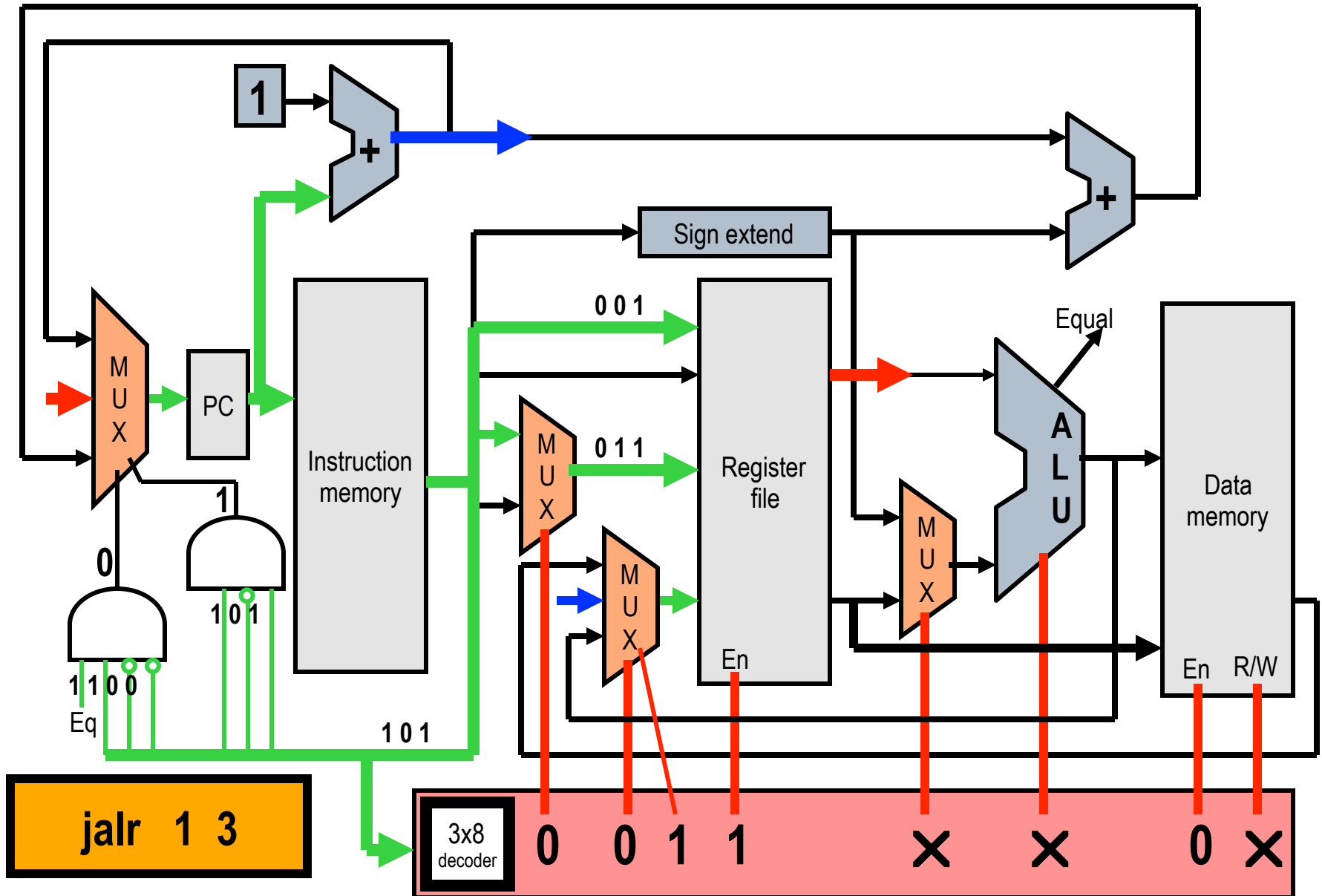
Executing a **JALR** Instruction on LC2Kx Datapath



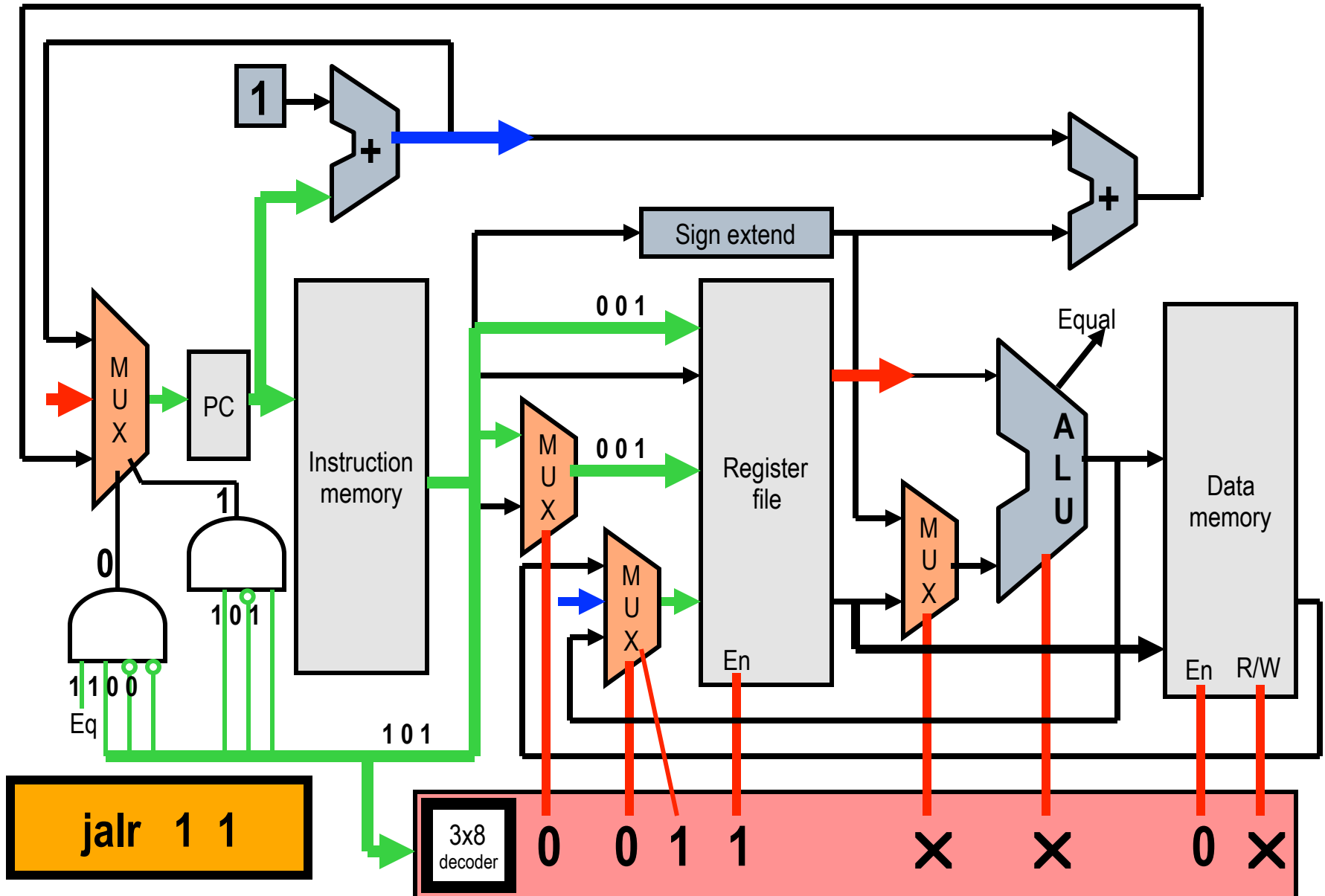What If $\text{regA} = \text{regB}$ for a JALR ?




Changes for a **JALR 1 1** Instruction

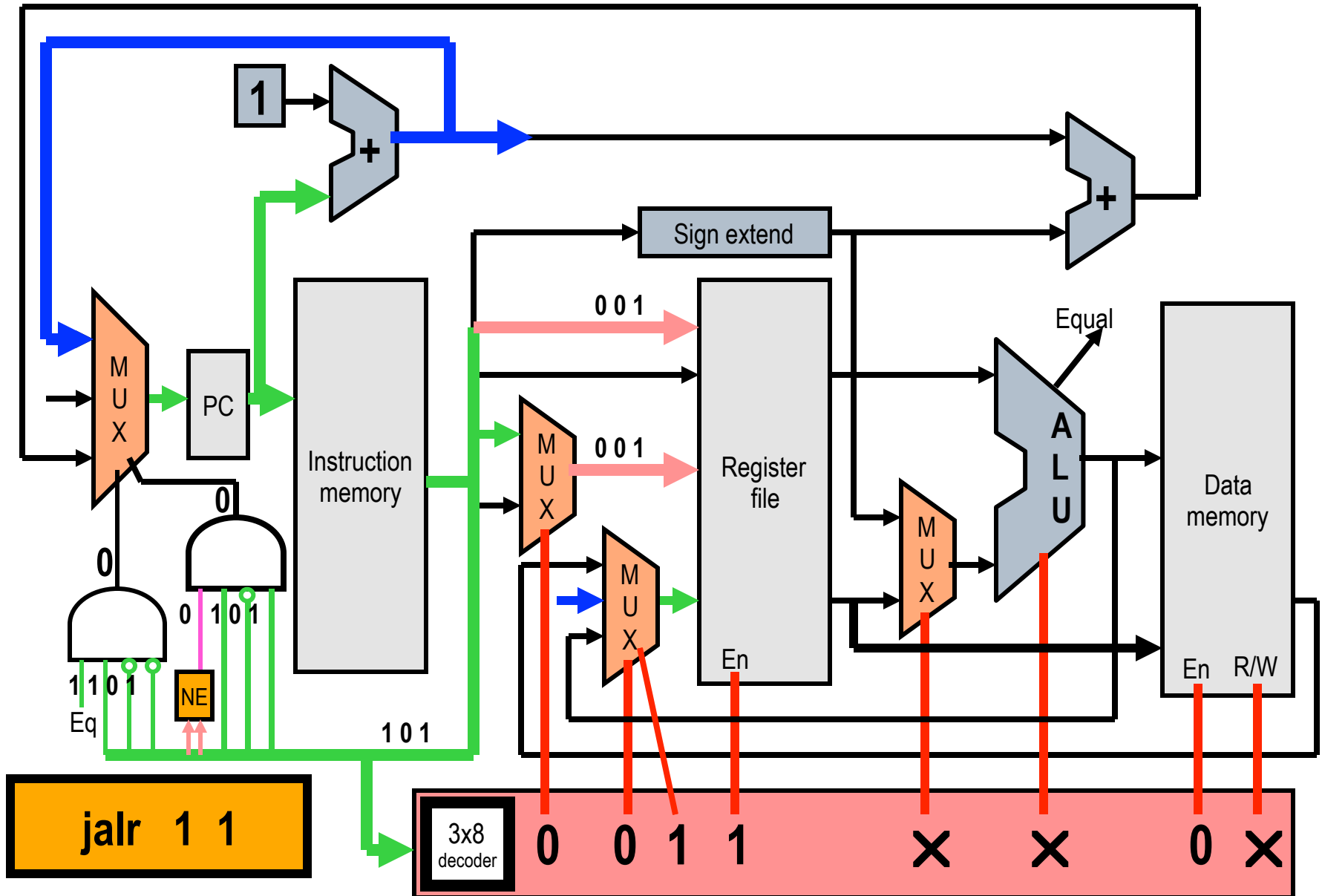

Class Problem

- ❑ Extend the single cycle datapath to perform the following operation
 - `cmov regA, regB, destR`
 - `destR = regA` (if `regB != 0`)
 - `PC = PC + 1`

Class Problem (continued)

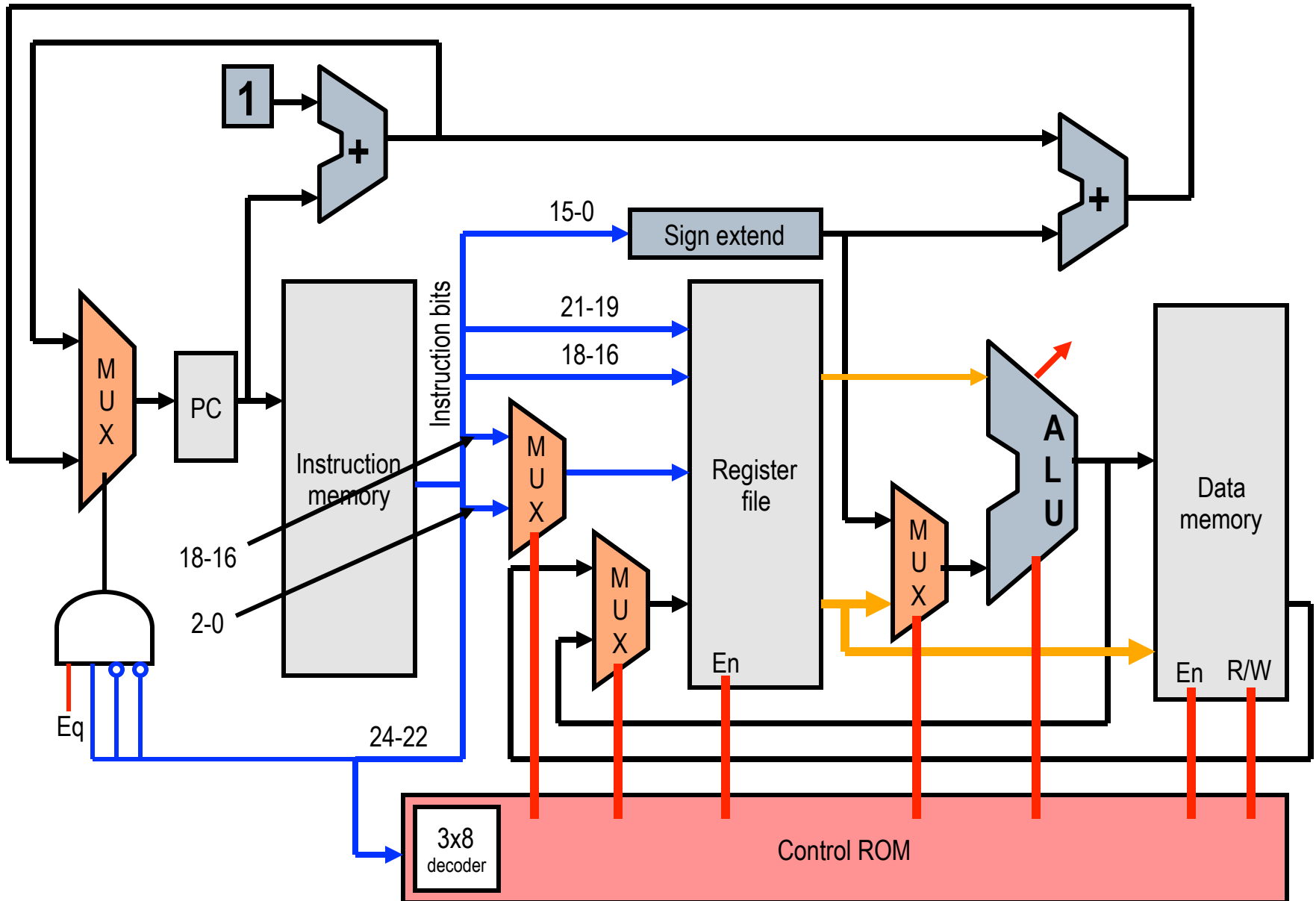

What's Wrong with Single Cycle?

- ❑ **All instructions run at the speed of the slowest instruction.**
- ❑ Adding a long instruction can hurt performance
 - What if you wanted to include multiply?
- ❑ You cannot reuse any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- ❑ No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

What's Wrong with Single Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

	Get Instr		read reg		ALU oper.		mem		write reg	
•	add:	2ns	+	1ns	+	2ns		+	1ns	= 6 ns
•	beq:	2ns	+	1ns	+	2ns				= 5 ns
•	sw:	2ns	+	1ns	+	2ns	+	2ns		= 7 ns
•	lw:	2ns	+	1ns	+	2ns	+	2ns	+	1ns = 8 ns

Computing Execution Time

❑ Assume: 100 instructions executed

- 25% of instructions are loads,
- 10% of instructions are stores,
- 45% of instructions are adds, and
- 20% of instructions are branches.

❑ Single-cycle execution:

= ??

❑ Optimal execution:

= ??

END OF EXAM1 MATERIAL